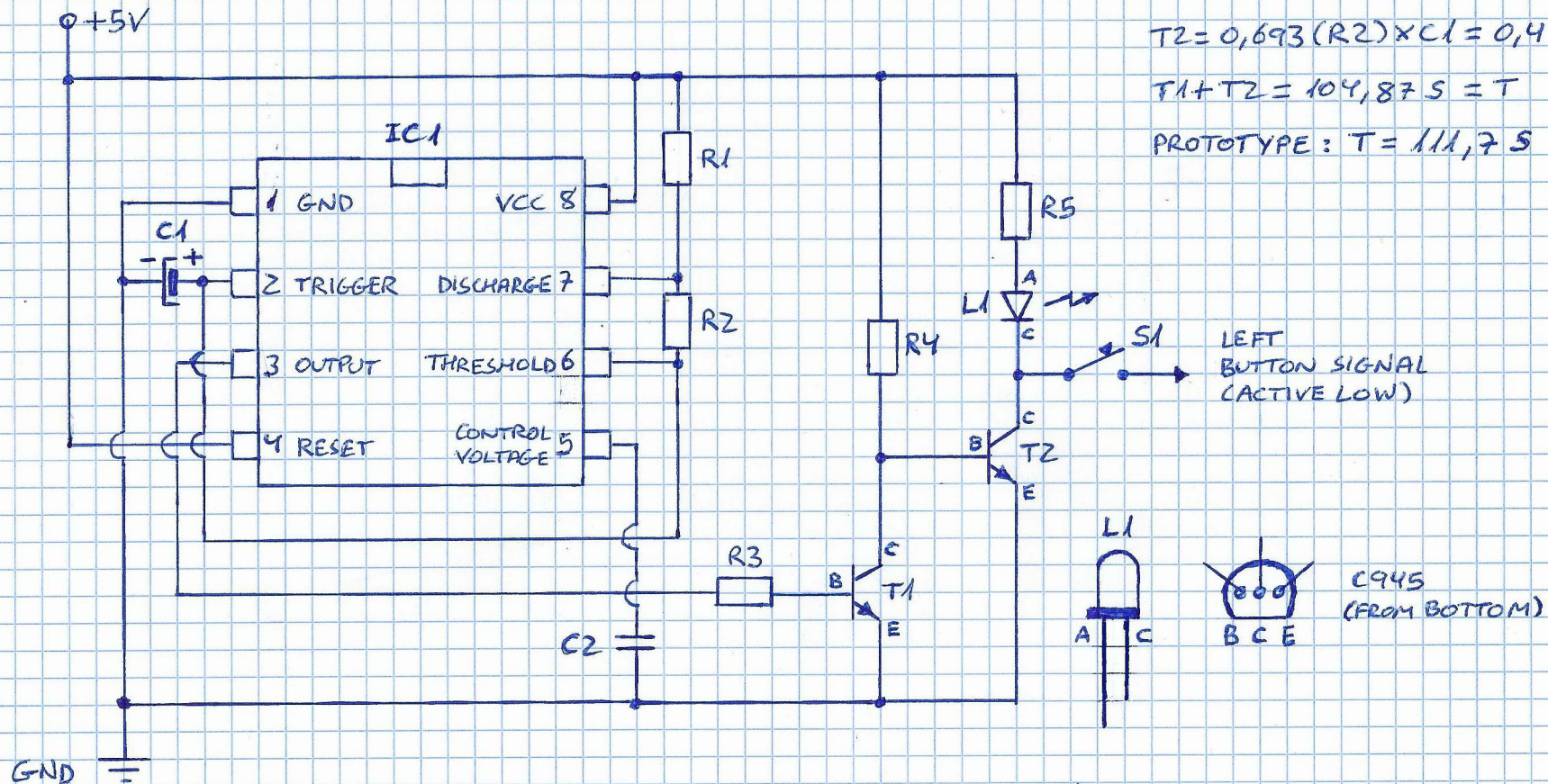


AUTOMATIC MOUSE LEFT KEY CLICKER



IC1 = NE555 INTEGRATED CIRCUIT

C1 = 100µF @ 16V ELECTROLYTIC CAPACITOR

C2 = 0,01µF CERAMIC CAPACITOR

T1 = T2 = C945 PNP TRANSISTOR

R1 = 1,5 MΩ @ 1/4 W RESISTOR

R2 = 6,8 KΩ @ 1/4 W RESISTOR

R3 = R4 = 1,2 KΩ @ 1/4 W RESISTOR

R5 = 150 Ω @ 1/4 W RESISTOR

L1 = 5MM LED

S1 = SWITCH, SINGLE CIRCUIT